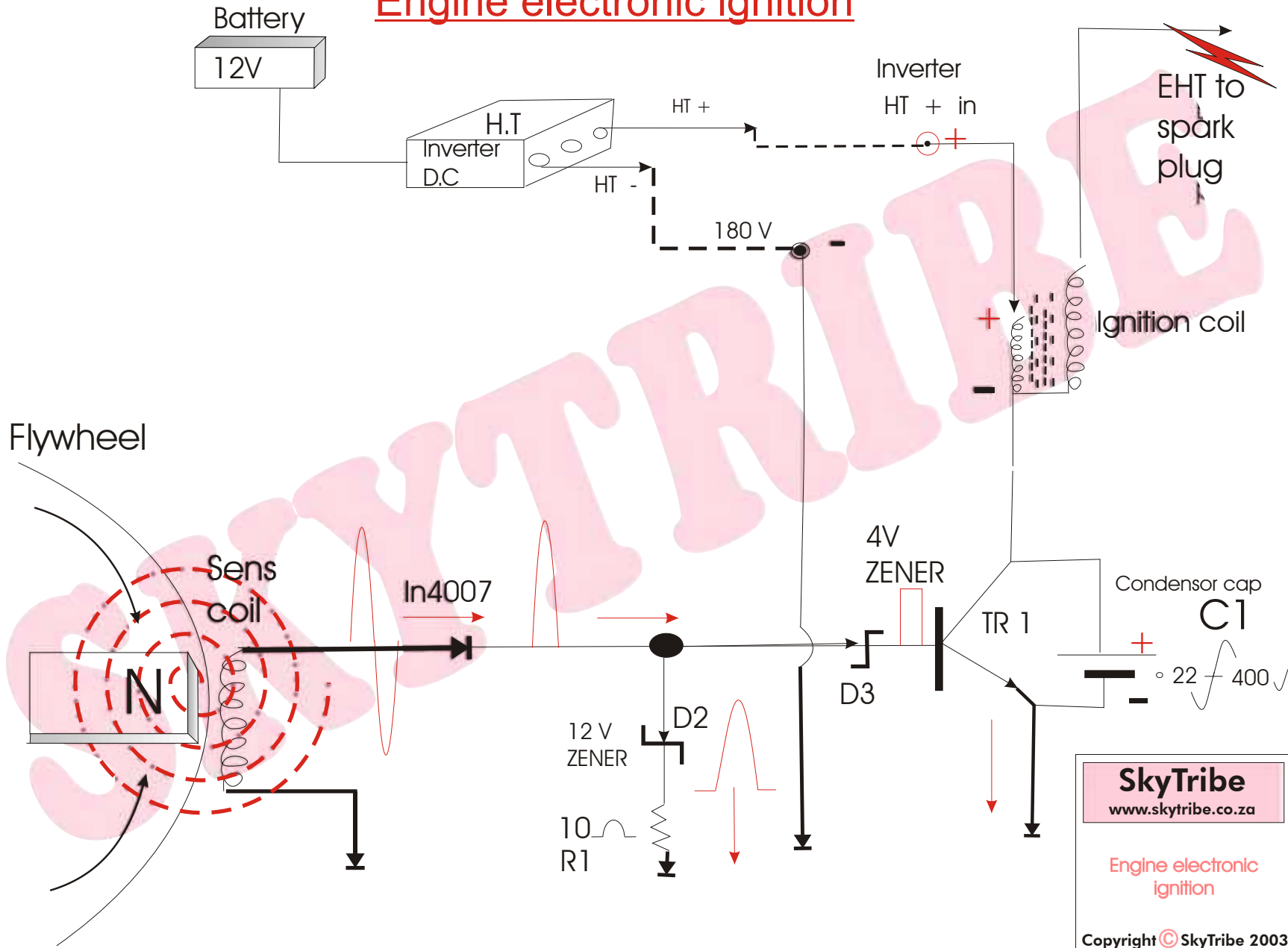


## Engine electronic ignition



### ENGINE ELECTRONIC IGNITION

The sensing coil generates an A.C pulse which is rectified to a + pulse at diode 1. The pulse passes through to diode 3 where the sudden cascade + voltage after zener D3 slams the transistor Tr1 on. The changed condenser capacitC1 is short circuited to earth by the switching on of Tr1. The charged field in the spark coil collapses the 180 volt E.H.T from the inverter and a super E.H.T spark results from the coil. D2 is an overload protector to protect the emitter base junction of the transistor. Any voltage above the 12V is shorted to earth via the load R1.

Beware the circuit generates a dangerous E.H.T of +- 97 KV. It was designed to fire an ignition circuit at a slow flick of the engine flywheel.

Designed by Keith Lehmann

**SkyTribe**

[www.skytribe.co.za](http://www.skytribe.co.za)

Engine electronic  
ignition

Copyright © SkyTribe 2003

**Please Note:** This is displayed to show the basics behind the ignition system. Before attempting such a circuit ensure it is thoroughly checked by a professional. **SkyTribe accepts NO responsibility for any damages, deaths or similar incidences WHATSOEVER.**